OPENRC Transmitter

OpenRC transmitter is stransmitter which was been primary designed for OpenRC f1, but can be used for all RC cars. Transmitter for forward moving use height sensors with which control speed of RC car. Speed is regulated with power of pressing to height sensor. For steering left and right transmitter use gyro sensor which detected steering transmitter and move wheels to the right position.

Hardware:

- 2x Arduino nano (https://www.ebay.com/itm/1-2PCS-Nano-V3-0-USB-ATmega328-16M-5V-Micro-Controller-CH340G-for-Arduino/192931268000?ssPageName=STRK%3AMEBIDX%3AIT&trksid=p2060353.m2749.l2649)
- GY-521 MPU-6050 Module 3 Axis Gyroscope (https://www.ebay.com/itm/High-Quality-MPU-6050-3-Axis-Accelerometer-Gyro-Sensor-Module-GY-521-Arduino-AU/282784754073?ssPageName=STRK%3AMEBIDX%3AIT&trksid=p2060353.m2749.l2649)
- 2x NRF24L01+PA+LNA SMA Antenna wireless transceiver
 (https://www.ebay.com/itm/NRF24L01-PA-LNA-SMA-Antenna-Wirele-Transceiver-communication-module-2-4G-1100-SE/132900720574?ssPageName=STRK%3AMEBIDX%3AIT& trksid=p2060353.m2749.l2649)
- 2x 8Pin Socket Adapter Board for NRF24L01 (https://www.ebay.com/itm/2PCS-Socket-Adapter-plate-Board-for-8Pin-NRF24L01-Wireless-Transceive-Module-51/263615734359?hash=item3d60b8e257:g:gSAAAOSw-uda1wk4)
- 50KG scale body load cell resistance strain weight sensor W/ HX711 AD module
 (https://www.ebay.com/itm/4Pcs-50KG-Body-Load-Cell-Resistance-Strain-Weight-Sensor-HX711-AD-Modules/264007214341?ssPageName=STRK%3AMEBIDX%3AIT&_trksid=p2060353.m2749.l2

 649)
- HX711 AD module (https://www.ebay.com/itm/Weighing-Sensor-AD-Module-Dual-channel-24-bit-A-D-Conversion-HX711-Shieding-CA-N/141975948937?hash=item210e6d0e89:g:vVYAAOxypNtSegO1)
- 2x Battery 7.4V (https://hobbyking.com/en_us/turnigy-nano-tech-180mah-2s-25c-lipoly-pack-compatible-losb0863-5pcs.html)
- 2x 3x8 screw
- 8x 3x12 screw

Connections:

1. Transmitter

NRF24L01+PA+LNA SMA (ANTENA):

ARDUINO NANO	SENSOR
5V	VCC
GND	GND
D12	M1
D11	M0
D13	SCK
D8	CSN
D7	CE

MPU-6050 (GYRO):

ARDUINO NANO	SENSOR
D2	INT
A4	SDA
A5	SCL
GND	GND
5V	VCC

HX711 AD (HEIGHT SENSOR RIGHT):


ARDUINO NANO	SENSOR
5V	VCC
GND	GND
DT	D3
SCK	D4
RED	A+
BLACK	E-
WHITE	E+
BLACK + 1K UPOR + WHITE + 1K UPOR	A-

HX711 AD (HEIGHT SENSOR LEFT):

ARDUINO NANO	SENSOR
5V	VCC
GND	GND
DT	D5
SCK	D6
RED	A+
BLACK	E-
WHITE	E+
BLACK + 1K UPOR + WHITE + 1K UPOR	A-

BATTERY:

ARDUINO NANO	BATTERY
GND	-
VCC	+

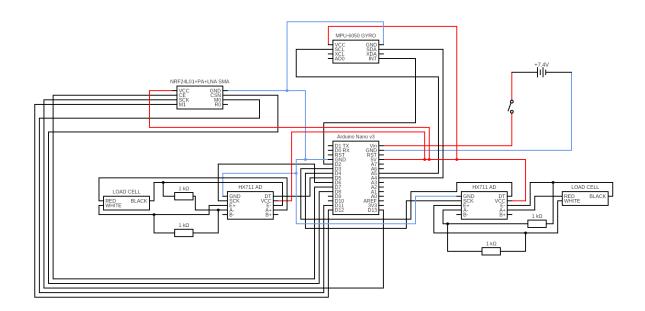

2. Receiver

NRF24L01+PA+LNA SMA (ANTENA):


ARDUINO NANO	SENSOR
5V	VCC
GND	GND
D12	M1
D11	M0
D13	SCK
D8	CSN
D7	CE

SERVO:

ARDUINO NANO	SENSOR
5V	RED
D9	ORANGE
GND	BROWN

ESC:

ARDUINO NANO	SENSOR
D10	WHITE
GND	BLACK
BLANK	RED

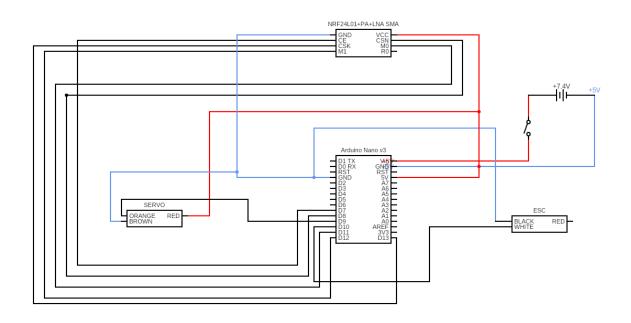

When you are connect all wires, then upload code to transmitter and receiver arduino uno.

When all is connected and code is uploaded to arduino, then is start to enjoy in driving your RC car.

If you like the model and want more models from me subscribe and support me on buymeacoffee (https://www.buymeacoffee.com/qfNog2M).